

Ohm's Law

Objective – to verify ohm's law.

Or

To study the dependence of potential difference (V) across a resistor on the current (I) passing through it and determine its resistance. Also, plot a graph between V and I.

Theory

The potential difference V across the metallic wire is directly proportional to the current flowing through it, provided its temperature is constant. This is known as Ohm's law.

$$V \propto I.$$

$\therefore V=IR$, where R is the resistance, which is constant for a given metallic wire.

What are the factors affecting resistance?

Following are the factors affecting resistance:

The nature of the resistor.

With an increase in length, the resistance also increases. So resistance of a wire is directly proportional to its length.

With an increase in the cross-sectional area, the resistance decreases. So resistance is inversely proportional to the cross-sectional area of the wire.

Apparatus Required

Following is the list of materials required for this experiment:

A battery

An insulated copper wire

A key

An ammeter


A voltmeter

A rheostat

A resistor

A piece of sandpaper

Circuit diagram

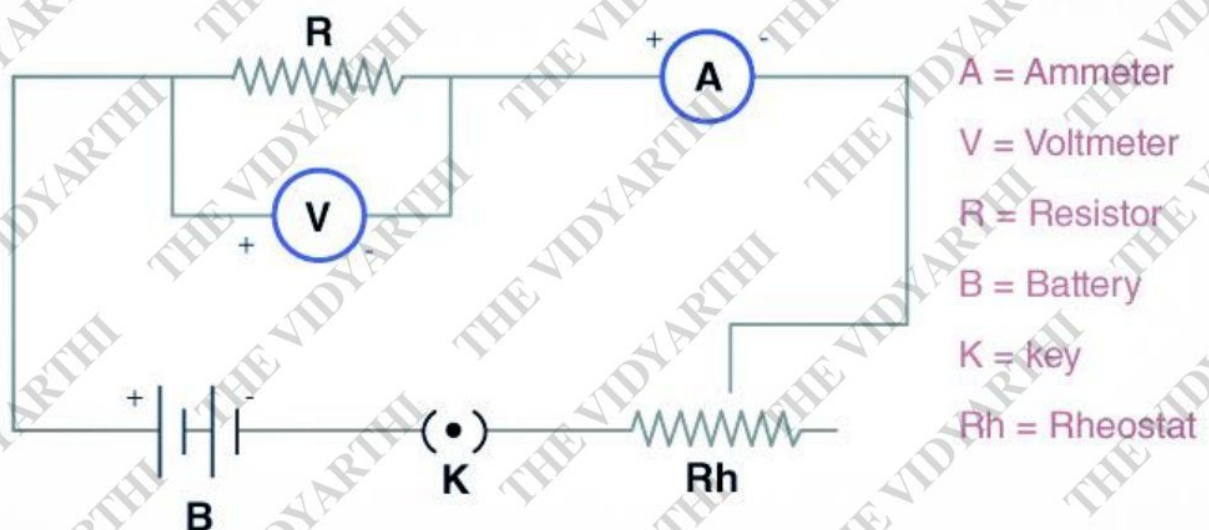

Procedure

Arrange the devices as shown in the circuit diagram.

Connect the devices with the connecting wires keeping the key open.

The positive terminal of the battery should be connected to the positive terminal of the ammeter.

Before connecting the voltmeter in the circuit, check for +ve and -ve terminals.

Check for ammeter and voltmeter reading once the circuit is connected and also adjust the slider of rheostat after inserting the key.

For current I and voltmeter V , record three different readings using a slider.

Record the observations in the observation table.

Using the formula $R=V/I$, calculate the resistance.

To plot the graph between V and I , take V on the x-axis and I on the y-axis.

For pure metals, resistance increases with an increase in temperature.

Observation Table


1. Least count of ammeter and voltmeter

Sl.no		Ammeter (A)	Voltmeter (V)
1	Range	0-0.5 A	0-0.1 V
2	Least count	0.01 A	0.01 V
3	Zero error (e)	0	0
4	Zero correction	0	0

2. For the reading of ammeter and voltmeter

Sl.no	Current in Ampere (I) (ammeter reading)		Potential difference in volts (V) (voltmeter reading)		Resistance $R = V/I (\Omega)$
	Observed	Corrected	Observed	Corrected	
1	0	0.02	0	0.04	$R_1 = 2\Omega$
2	0	0.03	0	0.06	$R_2 = 2\Omega$
3	0	0.04	0	0.08	$R_3 = 2\Omega$

Graph

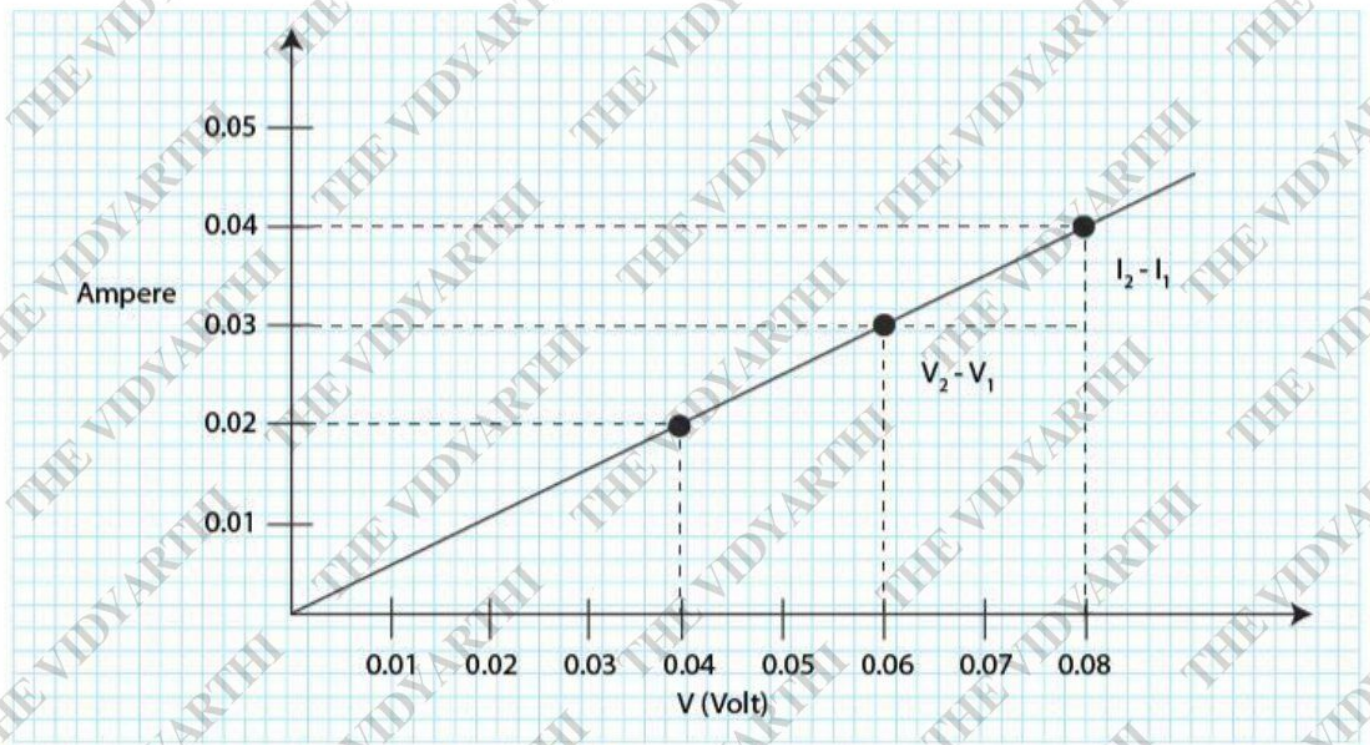

Graph between current and voltage

Conclusions

For all the three readings, the R-value is the same and constant.

The ratio of potential difference V and current I is the resistance of a resistor.

With the help of the graph between V and I , Ohm's law is verified as the plot is a straight line.

Viva Questions

Q1. Define electric current.

Ans: Electric current is defined as the rate of flow of electric charge in a conductor.

$$I = Q/T$$

Where,

I is the current in amperes

Q is the electric charge in coulombs

T is the time in seconds

Q2. What is the value of charge in 1 electron?

Ans: The value of charge in 1 electron is $1.6 \times 10^{-19} \text{C}$.

Q3. What is coulomb?

Ans: Coulomb is an SI unit of electric charge and is defined as the amount of charge present in 6.25×10^{18} electrons.

Q4. What is 1 volt?

Ans: If the work done in moving a charge of 1 Coulomb from one point to another is 1 Joule, then the potential difference between those two points is said to be 1 volt.

Q5. What is 1 ohm?

Ans: The resistance of a conductor is said to be 1 ohm if a current of 1 ampere flows through it when a potential difference of 1 volt is applied across its ends.